

Subject: Digital logic Fundamentals

Subject Code: (CS102S)

Class: I BSC (CS)

Staff –in-charge: C. Christy

PART-A (5 Marks)

1. Convert the following Decimal Number $(756.2)_{10}$ into Octal.
2. Convert the following Hexa Decimal Number $(10A7)_{16}$ into Binary.
3. Convert the Fractional Binary Number $(1011011.110)_2$ into $(?)_8, (?)_{16}$.
4. Find the 1's & 2's Complement for $(10101)_2$
5. Perform the following operation $1010 - 1011$ using 2's complement.
6. $7 - 5$ Subtract using 9's complement.
7. Multiply the numbers $(111)_2$ and $(101)_2$.
8. Prove $x.(x + y) = x$
9. Simplify the logical Expression $(x + y)(x' + z)(y + z)$
10. Explain about logic gates.
11. Prove: $AB + BC(B + C) = B(A + C)$
12. Explain EX-NOR gate with circuit diagram.
13. $F(A,B,C) = AB' + BC$ convert this into SOP
14. Define what is Max term?
15. $F(X,Y,Z) = \sum(0,2,3,5,7)$
16. Simplify the following Boolean Function $F(A,B,C,D) = \sum(0,1,5,8,9,10)$
17. $F(A,B,C) = \sum(0,4,7) + D(1,2,6)$
18. Simplify the function $Y = ABC' + ABC$ by k-map method.
19. Explain the classification of combinational logic circuit
20. Explain Half Subtractor.
21. Define what is Encoder?
22. Explain about RS Flip Flop.
23. Explain Binary-Up-Counter
24. What is T-Flip Flop?
25. Write the canonical form for $F(A,B,C) = \sum(0,2,3,5,7)$

PART-B (10 marks)

1. Explain Digital Computer with Neat diagram.
2. State and Explain about Number System.
3. Convert the following (i) $(AB.12)_{16}$ into Decimal [ii] $(750.12)_{10}$ into Octal.
4. ADD the Following Binary Numbers: $((111111)_2$ and $(1010101)_2$

5. Explain Basic Theorems and Rules of Boolean algebra?
6. Prove the Universality of NAND and NOR Gate
7. Prove De-Morgan's theorem.
8. Prove Distributive law: $A + (B \cdot C) = (A + B) \cdot C$
9. Draw Logic gate for $F(X, Y, Z) = (X + Y + Z') \cdot (X' Y Z')$
10. Explain Min Term & Max Term with Boolean values Table.
11. Prove: (i) $A \cdot (B \cdot C) = (A \cdot B) \cdot C$ (ii) $A \cdot (A + B) = A$
12. Find the Complement of $X(Y' + YZ) + YZ'$
13. Convert the following into Max Term $F(A,B,C)=(A+B') \cdot (B+C)$
14. Explain Various Types of k-maps in Detail.
15. Simplify using k-map $F(W,X,Y,Z)=(1,2,5,6,9,10,11,14,15)$
16. Explain Full Adder in Detail
17. What is BCD ADDER? How it is working?
18. Discuss about Binary Parallel Adder.
19. Explain in Detail about Multiplexors and De- Multiplexors.
20. Discuss about 3×8 Line Decoder
21. Explain about Clocked RS Flip Flop
22. Explain the Working of Master – Slave flip flop.
23. Discuss about JK flip flop.
24. State what is Counter? Discuss about Binary Ring Counter
25. Explain Asynchronous Counter with Clock Diagram